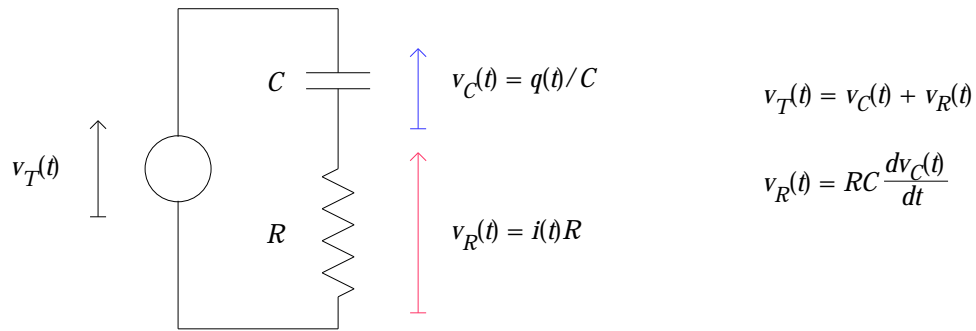


RC circuit; fast changes



Fast changes (high frequency): $T/2 \ll RC$; $f \gg 1/(2RC)$

