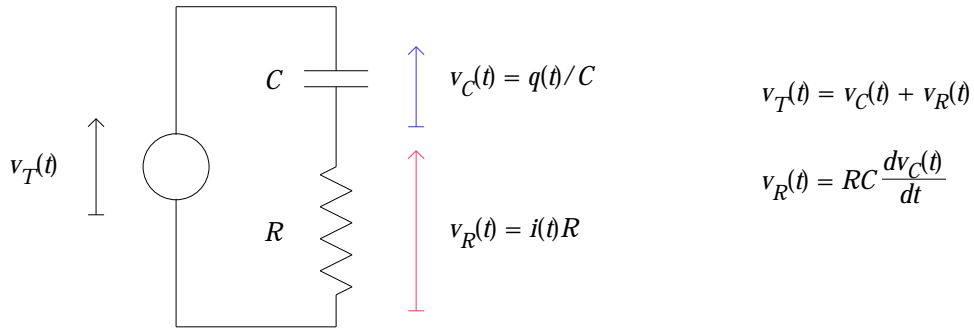


RC circuit; slow changes



Slow changes (low frequency): $T/2 \gg RC$; $f \ll 1/(2RC)$

